Name:_____   **Date:**_____

Circuits:_____
_____
_____

Complete Circuit	Incomplete Circuit
Explanation:_____ _____ _____	Explanation:_____ _____ _____